

**USP - ICMC - SSC
SCE 0703 (PISE) - 2o. Semestre 2008**

Disciplina de Projeto e Implementação de Sistemas Embarcados I

Prof. Fernando Santos Osório
Email: fosorio [at] { icmc. usp. br , gmail. com }
Web: <http://www.icmc.usp.br/~fosorio/>

Agenda:

- 1. Introdução: HDL - *Hardware Description Languages***
 - 1.1 Conceito de Linguagens de Descrição de Hardware**
 - 1.2 VHDL, Verilog, AHDL, SystemC, ...**
- 2. Conceitos Básicos de VHDL**
 - 2.1 Elementos Gerais da Linguagem**
Library (IEEE Std) / Entity / Architecture
 - 2.2 Componentes: Interfaces / Behavioral / Structural**
Test Benches / Language Elements
 - 2.3 Exemplos**
- 3. Ferramentas da Altera**
Quartus II - VHDL
ModelSim - VHDL
- 4. Discussão Final**

1. Introdução

HDL- *Hardware Description Language*

HDL - Conceitos e Origem

- Uma Linguagem de Descrição de Hardware, ou HDL, é uma classe de linguagem de computação e/ou programação usada para descrever de modo formal Circuitos Eletrônicos;
- Através de uma HDL podemos descrever o *funcionamento* de um circuito, seu *projeto* e sua *organização*, bem como é possível usar a HDL para desenvolver *testes e verificações* do circuito através de simulações;

HDL - Descrição de Circuitos Eletrônicos:

Portas Lógicas, Circuitos Combinatórios, Circuitos Integrados Digitais (Memórias, Decodificadores, Contadores, ULA, ...), Circuitos Analógicos, Microprocessadores, Processadores Dedicados, ...

1. Introdução

HDL - *Hardware Description Language*

HDL - Conceitos e Origem

- As primeiras linguagens HDL foram:
 - ISP (*Instruction Set Processor*), desenvolvida em Carnegie Mellon, e
 - KARL, desenvolvida na Univ. de Kaiserslautern, por volta de ~1977;
- ISP era similar a uma linguagem de programação de softwares usada para descrever relações entre entradas e saídas de um projeto;
- KARL incluía suporte para *VLSI chip floorplanning* e projetos de hardware;
- ABEL foi introduzida em 1983 pela Data-I/O. Era orientada ao projeto e descrição de PLDs (*Programmable logical devices*) e FSMs (*Finite state machines*);
- Verilog foi a 1a. linguagem HDL moderna, tendo sido introduzida em 1985 pela *Gateway Design Automation*, depois adquirida pela Cadence;
- VHDL foi criada por uma iniciativa do DoD (*US Department of Defense*) no final dos anos 80 com o suporte da IEEE, tornando-se um padrão para projetos => IEEE Standards 1076.1, 1076.2, 1076.3, 1164 / VHDL-4.0 2008
- SystemC, em 1999 é anunciada a *Open SystemC Initiative* (Synopsys)

1. Introdução

HDL - Hardware Description Language

HDL - Conceitos e Origem

Referências

ABEL - Advanced Boolean Expression Language (now owned by Xilinx Inc.)

Verilog - Verilog Ressources - <http://www.verilog.com/>

System Verilog - <http://www.eda.org/sv/> - <http://www.systemverilog.org/>

IEEE Standard 2001:

<http://ieeexplore.ieee.org/xpl/standardstoc.jsp?isnumber=20656&isYear=2001>

VHDL - Sites: <http://www.vhdl.org/>

<http://www.eda.org/> - <http://www.eda.org/rassp/vhdl/>

VHDL FAQ - <http://www.vhdl.org/comp.lang.vhdl/FAQ1.html>

SystemC - Site Oficial: <http://www.systemc.org/home>

Board of Members: <http://www.systemc.org/about/gallery/>

Veja também...

Wikipedia (en) - HDL, VHDL, Verilog, SystemC

5


Agosto 2008

1. Introdução

HDL - Hardware Description Language

HDL - Conceitos

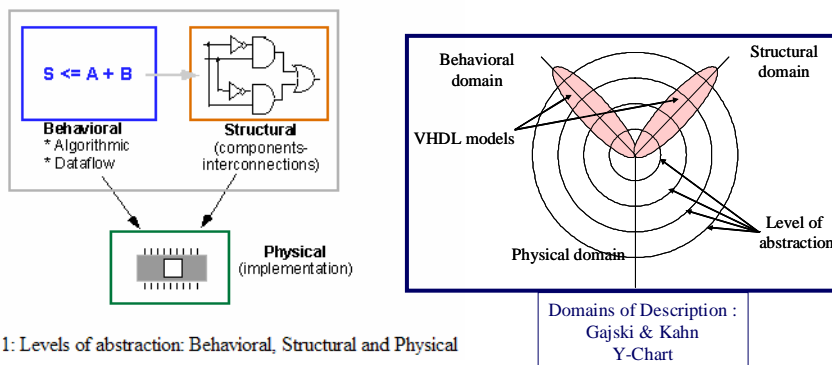Domínios de Descrição / Níveis de Abstração



6


Agosto 2008

1. Introdução

HDL - *Hardware Description Language*

HDL - Conceitos

 Domínios de Descrição / Níveis de Abstração



"Y-chart" due to
Gajski & Kahn

7


Agosto 2008

1. Introdução

HDL - *Hardware Description Language*

HDL - Conceitos

 Domínios de Descrição / Níveis de Abstração



"Y-chart" due to
Gajski & Kahn

8



Agosto 2008

1. Introdução

HDL - Hardware Description Language

HDL - Conceitos

  Domínios de Descrição / Níveis de Abstração




"Y-chart" due to
 Gajski & Kahn

1. Introdução

HDL - Hardware Description Language

HDL - Conceitos

 Domínios de Descrição / Níveis de Abstração




"Y-chart" due to
 Gajski & Kahn

1. Introdução

HDL - Hardware Description Language

HDL - Conceitos

 Domínios de Descrição / Níveis de Abstração



$S := ((\text{not}(A)) \text{ and } B) \text{ Or } (A \text{ and } (\text{not}(B)))$
 $C := A \text{ and } B$


“Y-chart” due to
 Gajski & Kahn

1. Introdução

HDL - Hardware Description Language

HDL - Conceitos

 Domínios de Descrição / Níveis de Abstração





“Y-chart” due to
 Gajski & Kahn

1. Introdução

HDL - Hardware Description Language

HDL - Conceitos

  Domínios de Descrição / Níveis de Abstração



“Y-chart” due to
Gajski & Kahn

13


Agosto 2008

1. Introdução

HDL - Hardware Description Language

HDL - Conceitos

Projeto usando HDL

 

Antes: Projeto Tradicional

14


Agosto 2008

1. Introdução

HDL - Hardware Description Language

HDL - Conceitos

Projeto usando HDL

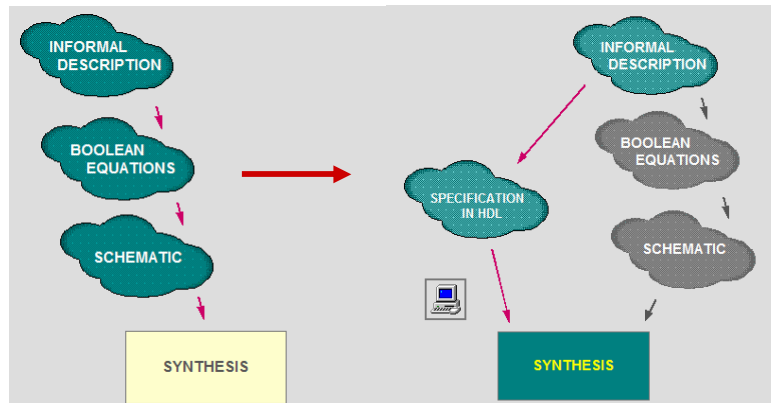

Depois: Projeto HDL

15


Agosto 2008

1. Introdução

HDL - Hardware Description Language

HDL - Conceitos

Projeto usando HDL

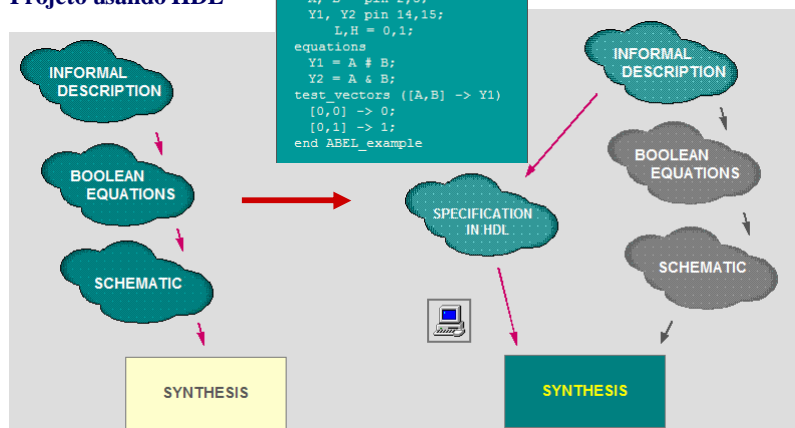

Depois: Projeto HDL

16


Agosto 2008

1. Introdução

HDL - *Hardware Description Language*

HDL - Conceitos

Projeto usando HDL

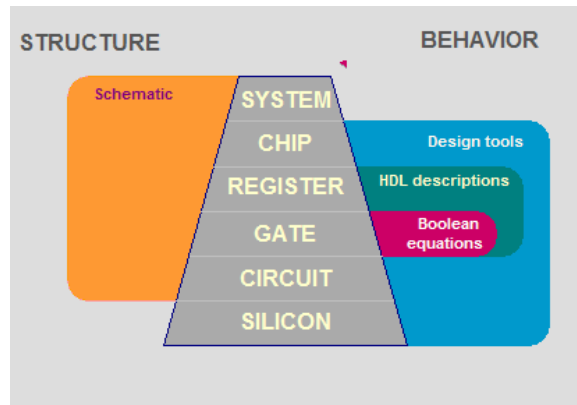

Depois: Projeto HDL

17


Agosto 2008

1. Introdução

HDL - *Hardware Description Language*

HDL - Conceitos

Projeto usando HDL

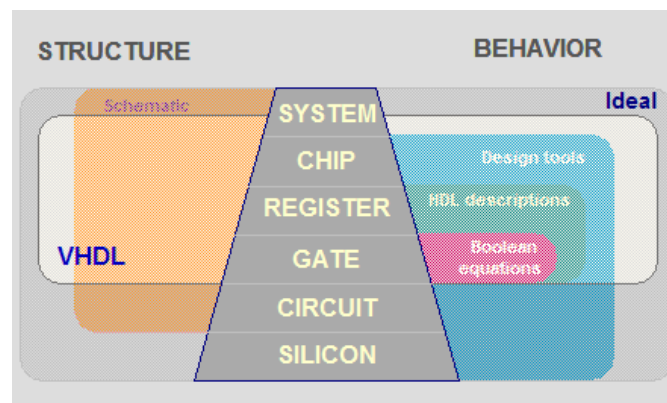

Depois: Projeto VHDL + Design Tools (EDA)

18


Agosto 2008

1. Introdução

HDL - Hardware Description Language

HDL - Conceitos

Projeto usando HDL

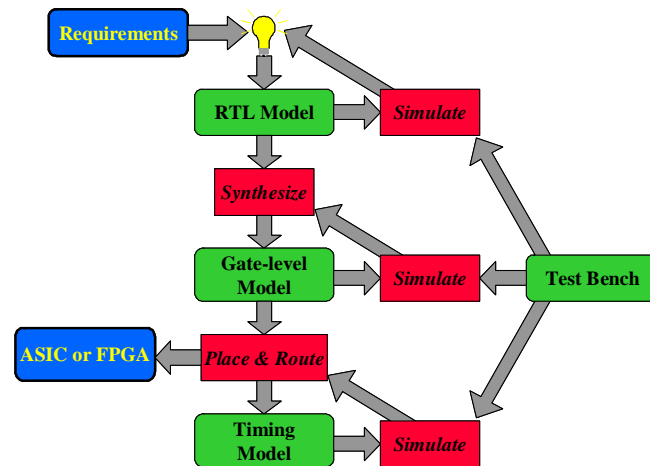

2. VHDL

VHSIC Hardware Description Language

VHDL - Conceitos Básicos

Siglas VHDL = VHSIC HDL

= VHSIC Hardware Description Language

VHSIC = Very High Speed Integrated Circuit

VHDL => Very High Speed Integrated Circuit Hardware Description Language

- Criada em meados dos anos 80 pelo militares americanos:

American Department of Defense "DoD";

- Objetivos:

> Descrição de alto nível (linguagem formal) de um sistema digital;

> Permitir a *simulação* de circuitos eletrônicos;

> Permitir a *síntese automática* de circuitos integrados (VLSI, ASIC, FPGA);

> Padronização (IEEE 1076-1993), Reuso, Prototipação

"Rapid Prototyping of Application Specific Circuits and Systems"

2. VHDL

VHDL - Histórico

- Early `70s: Initial discussions (ABEL)
- Late `70s: Definition of requirements
- Mid `82: Contract of development with IBM, Intermetrics and TI
- Mid `84: Version 7.2
- Mid `86: IEEE-Standard
- 1987: DoD adopts the standard -> IEEE.1076-1987
- Mid `88: Increasing support by CAE manufacturers
- Late `91: Revision
- 1993: New standard IEEE.1076-1993
- 1999: VHDL-AMS extension - IEEE 1076.1 (VHDL-AMS)
- IEEE Standards 1076.2, 1076.3, 1076.4, 1076.5 / 1164 STD Logic
- 2006: VHDL-3.0 October 2006
- 2008: VHDL-4.0 - IEEE.1076-2008 [<http://www.accellera.org/>]

21

Agosto 2008

2. VHDL


VHDL - Conceitos

* Requisitos da Linguagem VHDL:

Abstração / Modularidade / Concorrência (paralelismo) / Hierarquia


* Objetivos da Linguagem VHDL: Modelagem, Simulação e Síntese

Modelling

 


Z <= '1' when A='01'
else '0';

Simulation

 

Synthesis

 

22

Agosto 2008

VHDL - Conceitos

* Requisitos da Linguagem VHDL:

Abstração

- VHDL suporta descrições de componentes, bem como, de sistemas em diferentes níveis de abstração:
Gates, RTL, Processor-Memory Switch, Microprocessor and Systems;
- Portas e atrasos de componentes;
- Entradas e Saídas, Ciclos de Clock;
- Comportamento abstrato, sem noção de atrasos;
- Blocos: componentes vistos como "caixas pretas", apresentando uma visão externa da interface;
- Conexão de Macro-Blocos;
- Descrição: estrutural (*schematic*) ou comportamental (*algorithmic / data flow*).

23

Agosto 2008

VHDL - Conceitos

* Requisitos da Linguagem VHDL:

Modularidade

- Cada componente em VHDL é referido como uma entidade (entity) e tem uma interface claramente definida;
- A parte externa de um componente (interface) é chamada de "*entity declaration*";
- A parte interna de um componente (structure/behavior) é chamada de "*architecture declaration*";
- Podem haver múltiplas arquiteturas, inclusive em diferentes níveis de abstração, associadas com uma mesma entidade;

Concorrência Concurrent / Sequential - Behavior

- *Sequential Statements*: Procedural statements
- *Concurrent Statements*: Process statements and Component Instances

Algorithmic


Data Flow Style

24


Agosto 2008

2. VHDL

VHDL - Exemplo

 

Structural: Schematic / Gate

 


```

entity AND2 is
  port (a, b: in bit ;
        c : out bit);
end AND2;

architecture behavioral_2 of AND2 is
begin
  c <= a and b;
end behavioral_2;
  
```

VHDL

 

Behavioral:
Truth Table

B \ A	0	1
	0	1
0	0	0
1	0	1


25

Agosto 2008


2. VHDL

VHDL - Exemplo

Entity

 

 Entity - Describes only the interface (I/O)
 Circuit as a "Black-Box"



```

entity AND2 is
  port (a, b: in bit ;
        c : out bit);
end AND2;
  
```

```

entity HALF_ADDER is
  port (
    A, B: in bit;
    SUM, CARRY: out bit);
end HALF_ADDER;
  
```


26

Agosto 2008


2. VHDL

VHDL - Exemplo

Entity

 

 Entity - Describes only the interface (I/O)
Circuit as a "Black-Box"



```
entity AND2 is
  port (a, b: in bit ;
        c : out bit);
end AND2;
```

```
entity HALF_ADDER is
  port (
    A, B: in bit;
    SUM, CARRY: out bit);
end HALF_ADDER;
```


27
Agosto 2008

2. VHDL

VHDL - Exemplo


Architecture

 Structural / Behavioral Description
Architecture (internal)



$C \leq A \text{ and } B$

 Architecture: Describes circuit "function"
Structure / Behavior / Data Flow




```
architecture behavioral_2 of AND2 is
begin
  c <= a and b;
end behavioral_2;
```

```
architecture RTL of HALF_ADDER is
begin
  SUM <= A xor B;
  CARRY <= A and B;
end RTL;
```

28
Agosto 2008


2. VHDL

VHDL - Exemplo

 

```
entity AND2 is
    port (a, b: in bit ;
          c : out bit);
end AND2;

 architecture behavioral_2 of AND2 is
begin
    c <= a and b;
end behavioral_2;
```



```
entity HALF_ADDER is
    port (
        A, B: in bit;
        SUM, CARRY: out bit);
end HALF_ADDER;


architecture RTL of HALF_ADDER is
begin
    SUM <= A xor B;
    CARRY <= A and B;
end RTL;
```

29

Agosto 2008

2. VHDL

VHDL - Exemplo

 

```
library ieee;
use ieee.std_logic_1164.all;

entity AND2 is
    port (a, b: in std_logic;
          c : out std_logic);
end AND2;

architecture behavioral_2 of AND2 is
begin
    c <= a and b;
end behavioral_2;
```

Library: Usa a biblioteca padrão IEEE
Evite misturar BIT com STD_LOGIC

- BIT, BIT_VECTOR
 - Valores: "0" ou "1"
 - Atribuição de valor: bit_signal <= '0';
 - Nativos da linguagem VHDL, não precisam de declaração de biblioteca
- STD_LOGIC, STD_LOGIC_VECTOR
 - Valores: "0", "1", "-" (don't care), "Z" (alta impedância), "X" (indeterminado)
 - Biblioteca ieee
 - Declarações necessárias
 - LIBRARY
 - USE

30

Agosto 2008

2. VHDL

VHDL - Exemplo

Tipos de Sinais (I/O)

- **IN**: dados fluem para dentro da Entidade, que não pode escrever estes sinais
> Ex. Clock, entradas de controle, entradas unidirecionais de dados
- **OUT**: dados fluem para fora da Entidade, que não pode ler estes sinais.
> O modo OUT é usado quando a Entidade nunca lê estes dados
- **BUFFER**: dados fluem para fora da Entidade, que pode ler estes sinais, permitindo realimentação interna
> No entanto, o BUFFER não pode ser usado para entrada de dados
- **INOUT**: dados podem fluir para dentro ou para fora da Entidade
> Só deve ser usado se necessário
Ex. Barramento de dados bidirecional
> Design menos compreensível

Tipos de Dados

- **BIT, BIT_VECTOR**
 - Valores: "0" ou "1"
 - Atribuição de valor: `bit_signal <= '0';`
 - Nativos da linguagem VHDL, não precisam de declaração de biblioteca
- **STD_LOGIC, STD_LOGIC_VECTOR**
 - Valores: "0", "1", "Z" (alta impedância), "X" (indeterminado)
 - Biblioteca `ieee`
 - Declarações necessárias
* `LIBRARY`
* `USE`

Vetores Declaração:

```
bit_vector_signal : BIT_VECTOR(
    maximum_index DOWNT0 0 );
```

Vetores Atribuição:

```
bit_vector_signal(0) <= '1';
bit_vector_signal(0) <= bit_signal;
bit_vector_signal <= "0001";
```

31

Agosto 2008

2. VHDL - Linguagem

Linguagem VHDL - Componentes

Entity Declaration

The entity declaration defines the NAME of the entity and lists the input and output ports.


The general form is as follows:

```
entity NAME_OF_ENTITY is [ generic generic_declarations;]
    port (signal_names: mode type;
          signal_names: mode type;
          :
          signal_names: mode type);
end [NAME_OF_ENTITY] ;
```

-- Lines which starts with "--" are comments

-- Este é um comentário (termina no final da linha)

 -- A linguagem não é "case-sensitive" mas usualmente adota-se um estilo próprio



32

Agosto 2008

http://www.seas.upenn.edu/~ese201/vhdl/vhdl_primer.html

2. VHDL - Linguagem

Entity Declaration (cont.)

The NAME_OF_ENTITY is a user-selected identifier

* **Signal_names** consists of a comma separated list of one or more user-selected identifiers that specify external interface signals.

* **Mode:** is one of the reserved words to indicate the signal direction:

- > in – indicates that the signal is an input
- > out – indicates that the signal is an output of the entity whose value can only be read by other entities that use it.
- > buffer – indicates that the signal is an output of the entity whose value can be read inside the entity's architecture
- > inout – the signal can be an input or an output.

* **Type:** a built-in or user-defined signal type. Examples of types are:

bit, bit_vector, Boolean, character, std_logic, and std_ulogic.

- > bit – can have the value 0 and 1
- > bit_vector – is a vector of bit values (e.g. bit_vector (0 to 7))
- > std_logic, std_ulogic, std_logic_vector, std_ulogic_vector: can have 9 values to indicate the value and strength of a signal. Std_ulogic and std_logic are preferred over the bit or bit_vector types.
- > boolean – can have the value TRUE and FALSE
- > integer – can have a range of integer values
- > real – can have a range of real values
- > character – any printing character
- > time – to indicate time

33

Agosto 2008

2. VHDL - Linguagem


Entity Declaration (cont.)

Generic: generic declarations are optional and determine the local constants used for timing and sizing (e.g. bus widths) the entity. A generic can have a default value.

The syntax for a generic follows:

```
generic (
    constant_name: type [:=value] ;
    constant_name: type [:=value] ;
    :
    constant_name: type [:=value] );
```

 For the example of this figure, the entity declaration looks as follows:



-- comments: example of the buzzer circuit of the above figure

```
entity BUZZER is
    port (DOOR, IGNITION, SBELT: in std_logic;
          WARNING: out std_logic);
end BUZZER;
```

34


Agosto 2008

2. VHDL - Linguagem

Linguagem VHDL - Componentes

Architecture Declaration

 The architecture body specifies how the circuit operates and how it is implemented. As discussed earlier, an entity or circuit can be specified in a variety of ways, such as behavioral, structural (interconnected components), or a combination of the above. The architecture body looks as follows:



architecture architecture_name **of** NAME_OF_ENTITY **is**

```
-- Declarations
-- components declarations
-- signal declarations
-- constant declarations
-- function declarations
-- procedure declarations
-- type declarations
:
```

begin

```
-- Statements
:
```

end architecture_name;

35


Agosto 2008

2. VHDL - Linguagem

Linguagem VHDL - Componentes

Architecture Declaration

 The architecture body specifies how the circuit operates and how it is implemented. As discussed earlier, an entity or circuit can be specified in a variety of ways, such as **behavioral**, structural (interconnected components), or a combination of the above. The architecture body looks as follows:



architecture architecture_name **of** NAME_OF_ENTITY **is**

```
-- Declarations
-- components declarations
-- signal declarations
-- constant declarations
-- function declarations
-- procedure declarations
-- type declarations
:
```

begin

```
-- Statements
:
```

end architecture_name;

Behavioral model

The architecture body for the previous example, described at the behavioral level, is given below,

architecture behavioral **of** BUZZER **is**

begin

```
WARNING <= (not DOOR and IGNITION) or
            (not SBELT and IGNITION);
```

end behavioral;

36

Agosto 2008

2. VHDL - Linguagem

Linguagem VHDL - Componentes

Architecture Declaration: More Examples

```
library ieee;
use ieee.std_logic_1164.all;

entity AND2 is
    port (in1, in2: in std_logic;
          out1: out std_logic);
end AND2;

architecture behavioral_2 of AND2 is
begin
    out1 <= in1 and in2;
end behavioral_2;
```

Nota: observe que as atribuições "<=" são *comandos concorrentes*, ou seja, são executados ao mesmo tempo, onde sua ordem no texto não importa.

```
library ieee;
use ieee.std_logic_1164.all;

entity XNOR2 is
    port (A, B: in std_logic;
          Z: out std_logic);
end XNOR2;

architecture behavioral_xnor of XNOR2 is
    -- signal declaration (of internal signals X, Y)
    signal X, Y: std_logic;
begin
    X <= A and B;
    Y <= (not A) and (not B);
    Z <= X or Y;
end behavioral_xnor;
```

This implies that the statements are executed when one or more of the signals on the right hand side change their value (i.e. an event occurs on one of the signals).

37

Agosto 2008

2. VHDL - Linguagem


Linguagem VHDL - Componentes

Architecture Declaration

Architecture specifies how circuit operates and how it is implemented. Example of a **structural** (interconnected components) description.

```
architecture structural of BUZZER is
    -- Declarations
    component AND2
        port (in1, in2: in std_logic; out1: out std_logic);
    end component;
    component OR2
        port (in1, in2: in std_logic; out1: out std_logic);
    end component;
    component NOT1
        port (in1: in std_logic; out1: out std_logic);
    end component;
    -- declaration of signals used to interconnect gates
    signal DOOR_NOT, SBELT_NOT, B1, B2: std_logic;
```
 
```
begin
    -- Component instantiations statements
    U0: NOT1 port map (DOOR, DOOR_NOT);
    U1: NOT1 port map (SBELT, SBELT_NOT);
    U2: AND2 port map (IGNITION, DOOR_NOT, B1);
    U3: AND2 port map (IGNITION, SBELT_NOT, B2);
    U4: OR2 port map (B1, B2, WARNING);
end structural;
```



38

Agosto 2008

2. VHDL - Linguagem

Linguagem VHDL - Componentes

Architecture Declaration

Architecture specifies how circuit operates and how it is implemented. Example of a structural (interconnected components) description:

```
architecture structural of BUZZER is
    -- Declarations
    component AND2
        port (in1, in2: in std_logic; out1: out std_logic);
    end component;
    component OR2
        port (in1, in2: in std_logic; out1: out std_logic);
    end component;
    component NOT1
        port (in1: in std_logic; out1: out std_logic);
    end component;
    -- declaration of signals used to interconnect gates
    signal DOOR_NOT, SBELT_NOT, B1, B2: std_logic;
end structural;
```

```
begin
    -- Alternative association between the ports
    U0: NOT1 port map (in1 => DOOR, out1 => DOOR_NOT);
    U1: NOT1 port map (in1 => SBELT, out1 => SBELT_NOT);
    U2: AND2 port map (in1 => IGNITION, in2 => DOOR_NOT, out1 => B1);
    U3: AND2 port map (in1 => IGNITION, in2 => SBELT_NOT, B2);
    U4: OR2 port map (in1 => B1, in2 => B2, out1 => WARNING);
end structural;
```

```
begin
    -- Component instantiations statements
    U0: NOT1 port map (DOOR, DOOR_NOT);
    U1: NOT1 port map (SBELT, SBELT_NOT);
    U2: AND2 port map (IGNITION, DOOR_NOT, B1);
    U3: AND2 port map (IGNITION, SBELT_NOT, B2);
    U4: OR2 port map (B1, B2, WARNING);
end structural;
```

Nota: estes comandos também são concorrentes, não importando a ordem de sua declaração

39

Agosto 2008

2. VHDL - Linguagem

Linguagem VHDL - Componentes da Linguagem

Data Types defined in the Standard Package.

VHDL has several predefined types in the standard package.

To use this package one has to include the following clause:

```
library std, work;
use std.standard.all;
```

Cont...

Types defined in the Package <i>Standard</i> of the <i>std</i> Library		
Type	Range of values	Example
bit	'0', '1'	signal A: bit :=1;
bit_vector	an array with each element of type bit	signal INBUS: bit_vector(7 downto 0);
boolean	FALSE, TRUE	variable TEST: Boolean :=FALSE;
character	any legal VHDL character (see package standard); printable characters must be placed between single quotes (e.g. '#')	variable VAL: character :='\$';
file_open_kind*	read_mode, write_mode, append_mode	
file_open_status*	open_ok, status_error, name_error, mode_error	
integer	range is implementation dependent but includes at least $-(2^{31} - 1)$ to $+(2^{31} - 1)$	constant CONST1: integer :=129;
natural	integer starting with 0 up to the max specified in the implementation	variable VAR1: natural :=2;
positive	integer starting from 1 up to the max specified in the implementation	variable VAR2: positive :=2;
real*	floating point number in the range of -1.0×10^{38} to $+1.0 \times 10^{38}$ (can be implementation dependent. <i>Not supported by the Foundation synthesis program.</i>)	variable VAR3: real :=+64.2E12;
severity_level	note, warning, error, failure	

40

Agosto 2008

2. VHDL - Linguagem

VHDL

Type Conversion

Since VHDL is a strongly typed language one cannot assign a value of one data type to a signal of a different data type. In general, it is preferred to the same data types for the signals in a design, such as `std_logic` (instead of a mix of `std_logic` and bit types). Sometimes one cannot avoid using different types. To allow assigning data between objects of different types, one needs to convert one type to the other. Fortunately there are functions available in several packages in the ieee library, such as the `std_logic_1164` and the `std_logic_arith` packages. As an example, the `std_logic_1164` package allows the following conversions:

Conversions supported by std_logic_1164 package	
Conversion	Function
<code>std_logic</code> to bit	<code>to_bit(expression)</code>
<code>std_logic_vector</code> to bit_vector	<code>to_bitvector(expression)</code>
<code>std_logic_vector</code> to bit_vector	<code>to_bitvector(expression)</code>
bit to <code>std_logic</code>	<code>To_StdLogic(expression)</code>
bit_vector to <code>std_logic_vector</code>	<code>To_StdLogicVector(expression)</code>
bit_vector to <code>std_logic_vector</code>	<code>To_StdLogicVector(expression)</code>
<code>std_logic</code> to <code>std_logic_vector</code>	<code>To_StdLogicVector(expression)</code>
<code>std_logic</code> to <code>std_logic_vector</code>	<code>To_StdLogicVector(expression)</code>

41

Agosto 2008

The IEEE `std_logic_unsigned` and the IEEE `std_logic_arith` packages allow additional conversions such as from an integer to `std_logic_vector` and vice versa.

```
entity QUAD_NAND2 is
    port (A, B: in bit_vector(3 downto 0);
          out4: out std_logic_vector (3 downto 0));
end QUAD_NAND2;

architecture behavioral_2 of QUAD_NAND2 is
begin
    out4 <= to_StdLogicVector(A and B);
end behavioral_2;
```

2. VHDL - Linguagem

VHDL

Operators

7. Operators

VHDL supports different classes of operators that operate on signals, variables and constants. The different classes of operators are summarized below.

Class						
1. Logical operators	<code>and</code>	<code>or</code>	<code>nand</code>	<code>nor</code>	<code>xor</code>	<code>xnor</code>
2. Relational operators	<code>=</code>	<code>/=</code>	<code><</code>	<code><=</code>	<code>></code>	<code>>=</code>
3. Shift operators	<code>sll</code>	<code>srl</code>	<code>sla</code>	<code>sra</code>	<code>rol</code>	<code>ror</code>
4. Addition operators	<code>+</code>	<code>=</code>	<code>&</code>			
5. Unary operators	<code>+</code>	<code>-</code>				
6. Multiplying op.	<code>*</code>	<code>/</code>	<code>mod</code>	<code>rem</code>		
7. Miscellaneous op.	<code>**</code>	<code>abs</code>	<code>not</code>			

The order of precedence is the highest for the operators of class 7, followed by class 6 with the lowest precedence for class 1. Unless parentheses are used, the operators with the highest precedence are applied first. Operators of the same class have the same precedence and are applied from left to right in an expression. As an example, consider the following `std_logic_vector`s, X (= '010'), Y (= '10'), and Z ('10101'). The expression

`not X & Y xor Z rol 1`

is equivalent to `((not X) & Y) xor (Z rol 1) = ((101) & 10) xor (01011) = (10110) xor (01011) = 11101`. The xor is executed on a bit-per-bit basis.

42

Agosto 2008

2. VHDL - Linguagem

VHDL

Paralelismo: VHDL (Hw) versus Programação (Sw)

Sequential (Process)

x

Parallel (Concurrent)

* Parallel:

```
A <= B;
B <= A;
```

* Sequential:

```
Aux := A;
A := B;
B := Aux;
```

Signal x Variable

> Signal

```
Parallel:
A <= B;
B <= A;
```

> Variable

```
Sequential
Aux := A;
A := B;
B := Aux;
```

43

Agosto 2008

2. VHDL - Linguagem

Example of a process using Variables

```
architecture VAR of EXAMPLE is
    signal TRIGGER, RESULT: integer := 0;
begin
    process
        variable variable1: integer :=1;
        variable variable2: integer :=2;
        variable variable3: integer :=3;
    begin
        wait on TRIGGER;
        variable1 := variable2;
        variable2 := variable1 + variable3;
        variable3 := variable2;
        RESULT <= variable1 + variable2 + variable3;
    end process;
end VAR
```

Example of a process using Signals

```
architecture SIGN of EXAMPLE is
    signal TRIGGER, RESULT: integer := 0;
    signal signal1: integer :=1;
    signal signal2: integer :=2;
    signal signal3: integer :=3;
begin
    process
    begin
        wait on TRIGGER;
        signal1 <= signal2;
        signal2 <= signal1 + signal3;
        signal3 <= signal2;
        RESULT <= signal1 + signal2 + signal3;
    end process;
end SIGN;
```

Signal x Variable

44

Agosto 2008

2. VHDL - Linguagem

Example of a process using Variables	Signal x Variable
<pre> architecture VAR of EXAMPLE is signal TRIGGER, RESULT: integer := 0; begin process variable variable1: integer :=1; variable variable2: integer :=2; variable variable3: integer :=3; begin wait on TRIGGER; variable1 := variable2; variable2 := variable1 + variable3; variable3 := variable2; RESULT <= variable1 + variable2 + variab end process; end VAR; </pre>	<p>In the first case (using variable), the variables "variable1, variable2 and variable3" are computed sequentially and their values updated instantaneously after the TRIGGER signal arrives.</p> <p>Next, the RESULT, which is a signal, is computed using the new values of the variables and updated a time delta after TRIGGER arrives. This results in the following values (after a time TRIGGER): variable1 = 2 variable2 = 5 (=2+3) variable3 = 5.</p> <p>Since RESULT is a signal it will be computed at the time TRIGGER and updated at the time TRIGGER + Delta.</p> <p>Its value will be RESULT=12.</p>
Example of a process using Signals	
<pre> architecture SIGN of EXAMPLE is signal TRIGGER, RESULT: integer := 0; signal signal1: integer :=1; signal signal2: integer :=2; signal signal3: integer :=3; begin process begin wait on TRIGGER; signal1 <= signal2; signal2 <= signal1 + signal3; signal3 <= signal2; RESULT <= signal1 + signal2 + signal3; end process; end SIGN; </pre>	

2. VHDL - Linguagem

Example of a process using Variables	Signal x Variable
<pre> architecture VAR of EXAMPLE is signal TRIGGER, RESULT: integer := 0; begin process variable variable1: integer :=1; variable variable2: integer :=2; variable variable3: integer :=3; begin wait on TRIGGER; variable1 := variable2; variable2 := variable1 + variable3; variable3 := variable2; RESULT <= variable1 + variable2 + variab end process; end VAR; </pre>	<p>On the other hand, in the second example, using signals, the signals will be computed at the time TRIGGER.</p> <p>All of these signals are computed at the same time, using the old values of signal1, 2 and 3.</p> <p>All the signals will be updated at Delta time after the TRIGGER has arrived. Thus the signals will have these values:</p> <p>signal1= 2 signal2= 4 (=1+3) signal3= 2 and</p> <p>RESULT=6.</p>
Example of a process using Signals	
<pre> architecture SIGN of EXAMPLE is signal TRIGGER, RESULT: integer := 0; signal signal1: integer :=1; signal signal2: integer :=2; signal signal3: integer :=3; begin process begin wait on TRIGGER; signal1 <= signal2; signal2 <= signal1 + signal3; signal3 <= signal2; RESULT <= signal1 + signal2 + signal3; end process; end SIGN; </pre>	

2. VHDL - Linguagem

VHDL

Behavioral Modeling: Sequential Statements

VHDL provides means to represent digital circuits at different levels of representation of abstraction, such as the behavioral and structural modeling. Here we will discuss different constructs for describing the behavior of components and circuits in terms of sequential statements.

The basis for sequential modeling is the process construct.

The process construct allows us to model complex digital systems, in particular sequential circuits.

Syntax:

```
[process_label:] process [ (sensitivity_list) ] [is]  
[ process_declarations]
```

begin

list of sequential statements such as:

- signal assignments
- variable assignments
- case statement
- exit statement
- if statement
- loop statement
- next statement
- null statement
- procedure call
- wait statement

end process [process_label];

47

Agosto 2008

2. VHDL - Linguagem

VHDL

Behavioral Modeling: Sequential Statements

Syntax:

```
[process_label:] process [ (sensitivity_list) ] [is]  
[ process_declarations]
```

begin

list of sequential statements such as:

- signal assignments
- variable assignments
- case statement
- exit statement
- if statement
- loop statement
- next statement
- null statement
- procedure call
- wait statement

end process [process_label];

Example of a positive edge-triggered D flip-flop with asynchronous clear input follows.

```
library ieee;  
use ieee.std_logic_1164.all;  
  
entity DFF_CLEAR is  
  port (CLK, CLEAR, D : in std_logic;  
        Q : out std_logic);  
end DFF_CLEAR;  
  
architecture BEHAV_DFF of DFF_CLEAR is  
  begin  
    DFF_PROCESS: process (CLK, CLEAR)  
      begin  
        if (CLEAR = '1') then  
          Q <= '0';  
        elsif (CLK'event and CLK = '1') then  
          Q <= D;  
        end if;  
      end process;  
  end BEHAV_DFF;
```

48


Agosto 2008

2. VHDL - Linguagem

VHDL

Behavioral Modeling: Sequential Statements

 Example: Full-Adder composed of 2 Half-Adders



Full Adder composed of two Half Adders, modeled with two processes P1 and P2.

Example of Sequential Execution: P1 => P2

HA1

$S_ha = (A \text{ xor } B)$

$C_ha = A.B$

HA2

$Sum = (A \text{ xor } B) \text{ xor } Cin = S_ha \text{ xor } Cin$

$Cout = (A \text{ xor } B).Cin + A.B = S_ha.Cin + C_ha$

```
library ieee;
use ieee.std_logic_1164.all;

entity FULL_ADDER is
    port (A, B, Cin : in std_logic;
          Sum, Cout : out std_logic);
end FULL_ADDER;

architecture BEHAV_FA of FULL_ADDER is
    signal int1, int2, int3: std_logic;
begin
    -- Process P1 that defines the first half adder
    P1: process (A, B)
        begin
            int1<= A xor B;
            int2<= A and B;
        end process;

    -- Process P2 defines the second half adder and the OR
    P2: process (int1, int2, Cin)
        begin
            Sum <= int1 xor Cin;
            int3 <= int1 and Cin;
            Cout <= int2 or int3;
        end process;
    end BEHAV_FA;
```

49


Agosto 2008

2. VHDL - Linguagem

VHDL

Hierarchical Design

 Example: 4-bit adder consisting of full adder modules



-- Example of a four bit adder

```
library ieee;
use ieee.std_logic_1164.all;
-- definition of a full adder
entity FULLADDER is
    port (a, b, c: in std_logic;
          sum, carry: out std_logic);
end FULLADDER;
```

```
architecture fulladder_behav of FULLADDER is
begin
    sum <= (a xor b) xor c ;
    carry <= (a and b) or (c and (a xor b));
end fulladder_behav;
```

-- 4-bit adder

```
library ieee;
use ieee.std_logic_1164.all;

entity FOURBITADD is
    port (a, b: in std_logic_vector(3 downto 0);
          Cin : in std_logic;
          sum: out std_logic_vector (3 downto 0);
          Cout, V: out std_logic);
end FOURBITADD;

architecture fouradder_structure of
    FOURBITADD is
    ...
end fouradder_structure;
```

50

Agosto 2008

```


-- 4-bit adder
library ieee;
use ieee.std_logic_1164.all;

entity FOURBITADD is
  port (a, b: in std_logic_vector(3 downto 0);
        Cin: in std_logic;
        sum: out std_logic_vector(3 downto 0);
        Cout, V: out std_logic);
end FOURBITADD;

architecture fouradder_structure of
  FOURBITADD is
    signal c: std_logic_vector(4 downto 0);
    component FULLADDER
      port (a, b, c: in std_logic;
            sum, carry: out std_logic);
    end component;
  begin
    FA0: FULLADDER
      port map (a(0), b(0), C(0), sum(0), c(1));
    FA1: FULLADDER
      port map (a(1), b(1), C(1), sum(1), c(2));
    FA2: FULLADDER
      port map (a(2), b(2), C(2), sum(2), c(3));
    FA3: FULLADDER
      port map (a(3), b(3), C(3), sum(3), c(4));
    V <= c(3) xor c(4);
    Cout <= c(4);
  end fouradder_structure;

```

2. VHDL - Linguagem

 

```

-- Example of a four bit adder
library ieee;
use ieee.std_logic_1164.all;
-- definition of a full adder
entity FULLADDER is
  port (a, b, c: in std_logic;
        sum, carry: out std_logic);
end FULLADDER;

architecture fulladder_behav of FULLADDER is
begin
  sum <= (a xor b) xor c ;
  carry <= (a and b) or (c and (a xor b));
end fulladder_behav;

```

2. VHDL - Linguagem

VHDL Test Benches

- Testing a design by simulation
- Use a **test bench** model
 - An architecture body that includes an instance of the design under test
 - Applies sequences of test values to inputs
 - Monitors values on output signals
 - either using simulator
 - or with a process that verifies correct operation

2. VHDL - Linguagem

VHDL

Test Bench Example

```
entity test_bench is
end entity test_bench;

architecture test_reg4 of test_bench is
    signal d0, d1, d2, d3, en, clk, q0, q1, q2, q3 : bit;
begin
    dut : entity work.reg4(behav)
        port map ( d0, d1, d2, d3, en, clk, q0, q1, q2, q3 );
    stimulus : process is
    begin
        d0 <= '1'; d1 <= '1'; d2 <= '1'; d3 <= '1'; wait for 20 ns;
        en <= '0'; clk <= '0'; wait for 20 ns;
        en <= '1'; wait for 20 ns;
        clk <= '1'; wait for 20 ns;
        d0 <= '0'; d1 <= '0'; d2 <= '0'; d3 <= '0'; wait for 20 ns;
        en <= '0'; wait for 20 ns;
        ...
        wait;
    end process stimulus;
end architecture test_reg4;
```

53

Agosto 2008

2. VHDL - Linguagem

VHDL Test Benches

Regression Testing

- Test that a refinement of a design is correct
 - that lower-level structural model does the same as a behavioral model
- Test bench includes two instances of design under test
 - behavioral and lower-level structural
 - stimulates both with same inputs
 - compares outputs for equality
- Need to take account of timing differences

54

Agosto 2008

2. VHDL - Linguagem

VHDL

Regression

Test

Example

```
architecture regression of test_bench is
  signal d0, d1, d2, d3, en, clk : bit;
  signal q0a, q1a, q2a, q3a, q0b, q1b, q2b, q3b : bit;
begin
  dut_a : entity work.reg4(struct)
    port map ( d0, d1, d2, d3, en, clk, q0a, q1a, q2a, q3a );
  dut_b : entity work.reg4(behav)
    port map ( d0, d1, d2, d3, en, clk, q0b, q1b, q2b, q3b );
  stimulus : process is
  begin
    d0 <= '1'; d1 <= '1'; d2 <= '1'; d3 <= '1'; wait for 20 ns;
    en <= '0'; clk <= '0'; wait for 20 ns;
    en <= '1'; wait for 20 ns;
    clk <= '1'; wait for 20 ns;
    ...
    wait;
  end process stimulus;
  ...
```

Cont...

55

Agosto 2008

2. VHDL - Linguagem

VHDL

Regression

Test

Example

```
...
verify : process is
begin
  wait for 10 ns;
  assert q0a = q0b and q1a = q1b and q2a = q2b and q3a = q3b
    report "implementations have different outputs"
    severity error;
  wait on d0, d1, d2, d3, en, clk;
end process verify;
end architecture regression;
```

56

Agosto 2008

2. VHDL - Linguagem

VHDL

Exemplos

> Ver referências...

Sugestão de Atividade

> Tutorial Interativo da ALDEC sobre VHDL

2. VHDL - Linguagem

VHDL x Verilog*

VHDL	Verilog
All abstraction levels	All abstraction levels
Complex grammar	Easy language
Describe a system (everything)	Describe a digital system
Lots of data types	Few data types
User-defined package & library	No user-defined packages
Full design parameterization	Simple parameterization
Easier to handle large designs	
Very consistent language. Code written and simulated in one simulator will behave exactly the same in another simulator. E.g. strong typing rules.	Less consistent language. If you don't follow some adhoc methodology for coding styles, you will not get it right.
* Comparison according to: Dr. Gábor Hosszú http://nimrud.eet.bme.hu/cae/ppt/2vhdl/1intro.ppt	It executes differently on different platforms unless you follow some adhoc coding rules.

2. VHDL - Linguagem

VHDL x Verilog*

- It does seem that **Verilog** is easier for designing at the gate-level, but that people who do higher level simulations express a preference for **VHDL**
- VHDL places constraints on evaluation order that limit the optimizations that can be performed
 - Verilog allows the simulator greater freedom
 - For example, multiple levels of zero-delay gates can be collapsed into a single super-gate evaluation in Verilog
 - VHDL requires preserving the original number of delta cycles of delay in propagating through those levels

VHDL	Verilog
In Europe the VHDL is the most popular language	
Based on Pascal language	Based on C language
Most FPGA design in VHDL	Most ASIC design in Verilog

59

Agosto 2008

* Comparison according to: Dr. Gábor Hosszú - <http://nimrud.eet.bme.hu/cae/ppt/2vhdl/1intro.ppt>

HDL / VHDL Hardware Description Language

HDL - Referências

Aldec

Tutorials: VHDL, Verilog, SystemC
Software : Active-HDL Student Edition (Free)
<http://www.aldec.com/Downloads/default.aspx>

HDL - Hardware Description Languages
History and Languages
http://en.wikipedia.org/wiki/Hardware_description_language

VHDL: On-Line Material

> Introdução à Linguagem VHDL - Luís Henrique Costa / UFRJ
<http://www.gta.ufrj.br/ensino/EEL480/Introducao-VHDL.ppt>

> VHDL Quick Start - Peter Ashenden / Univ. of Adelaide
<http://www.ashenden.com.au/designers-guide/VHDL-quick-start.pdf>

> Introduction to VHDL - M. Balakrishnan / IIT Delhi
[http://www.cse.iitd.ernet.in/~mbala/csl316/slides/ \(Sec6.ppt\)](http://www.cse.iitd.ernet.in/~mbala/csl316/slides/ (Sec6.ppt))

> VHDL Tutorial - ESE201 / UPENN
http://www.seas.upenn.edu/~ese201/vhdl/vhdl_primer.html

> VHDL Tutorial On-Line
<http://www.vhdl-online.de/~vhdl/tutorial/>

Continua...

60

Agosto 2008

HDL - Referências

VHDL: On-Line Material

- > VHDL Class
http://web.cecs.pdx.edu/~mperkows/CLASS_VHDL/index.html
 - > RASSP - DARPA Rapid Prototyping of Application Specific Signal Processors (RASSP)
<http://www.eda.org/rassp/>
 - > VHDL Tutorial: Learn by Example - Weijun Zhang
<http://esd.cs.ucr.edu/labs/tutorial/>
 - > VHDL Faq
<http://www.vhdl.org/comp.lang.vhdl/FAQ1.html>
- => Disciplina SCE 0703 - Ver Material Complementar! <http://www.icmc.usp.br/~fosorio/>

VHDL: Referências

- > Digital Fundamental with VHDL - Floyd (Biblioteca)
- > Projeto e Prototipação de Sistemas Digitais - Luigi Carro (Biblioteca)
- > VHDL Intro - Eduardo Simões

That's all folks!



INFORMAÇÕES SOBRE A DISCIPLINA

USP - Universidade de São Paulo - São Carlos, SP
ICMC - Instituto de Ciências Matemáticas e de Computação
SSC - Departamento de Sistemas de Computação

Prof. Fernando Santos OSÓRIO

Web institucional: <http://www.icmc.usp.br/ssc/>

Página pessoal: <http://www.icmc.usp.br/~fosorio/>

E-mail: [fosorio \[at\] icmc. usp. br](mailto:fosorio@icmc.usp.br) ou [fosorio \[at\] gmail. com](mailto:fosorio@gmail.com)

Disciplina de Proj. e Implementação de Sistemas Embarcados I

Ferramentas: Altera - Quartus, NIOS II, Cyclone Dev-Kit

Web disciplina: [Http://www.icmc.usp.br/~fosorio/](http://www.icmc.usp.br/~fosorio/)

> Programa, Material de Aulas, Critérios de Avaliação,

> Material de Apoio, Trabalhos Práticos